
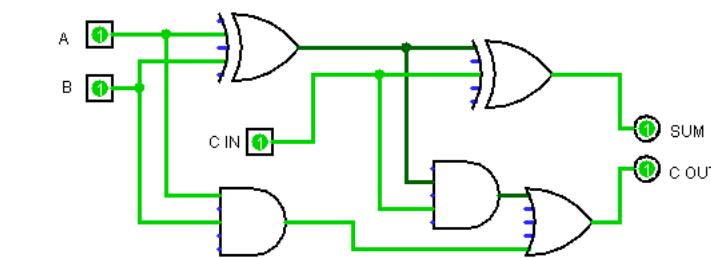
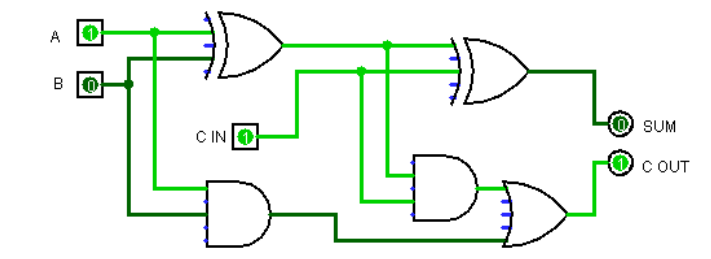
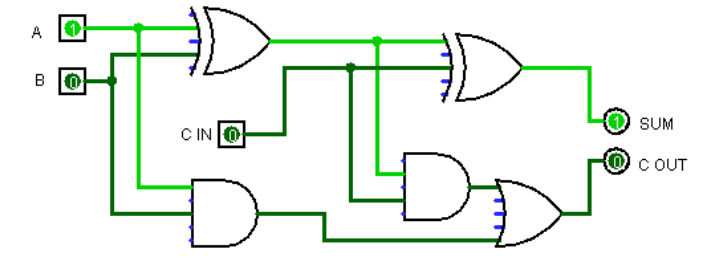
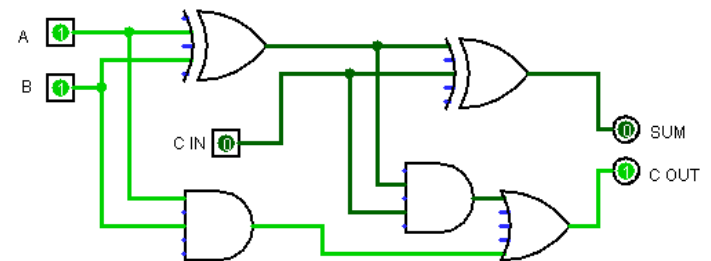



Project: Full Adder
 Brandon Ackerman
 11/12/20

YouTube Video for TinkerCad Circuit: https://youtu.be/aPk6PJ21C_g




A	B	C in	SUM	C out
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
1	1	0	0	1
0	0	1	1	0
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

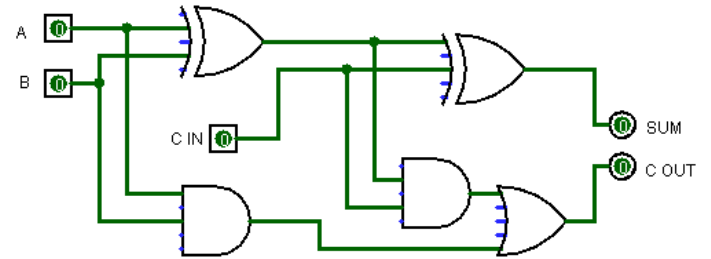

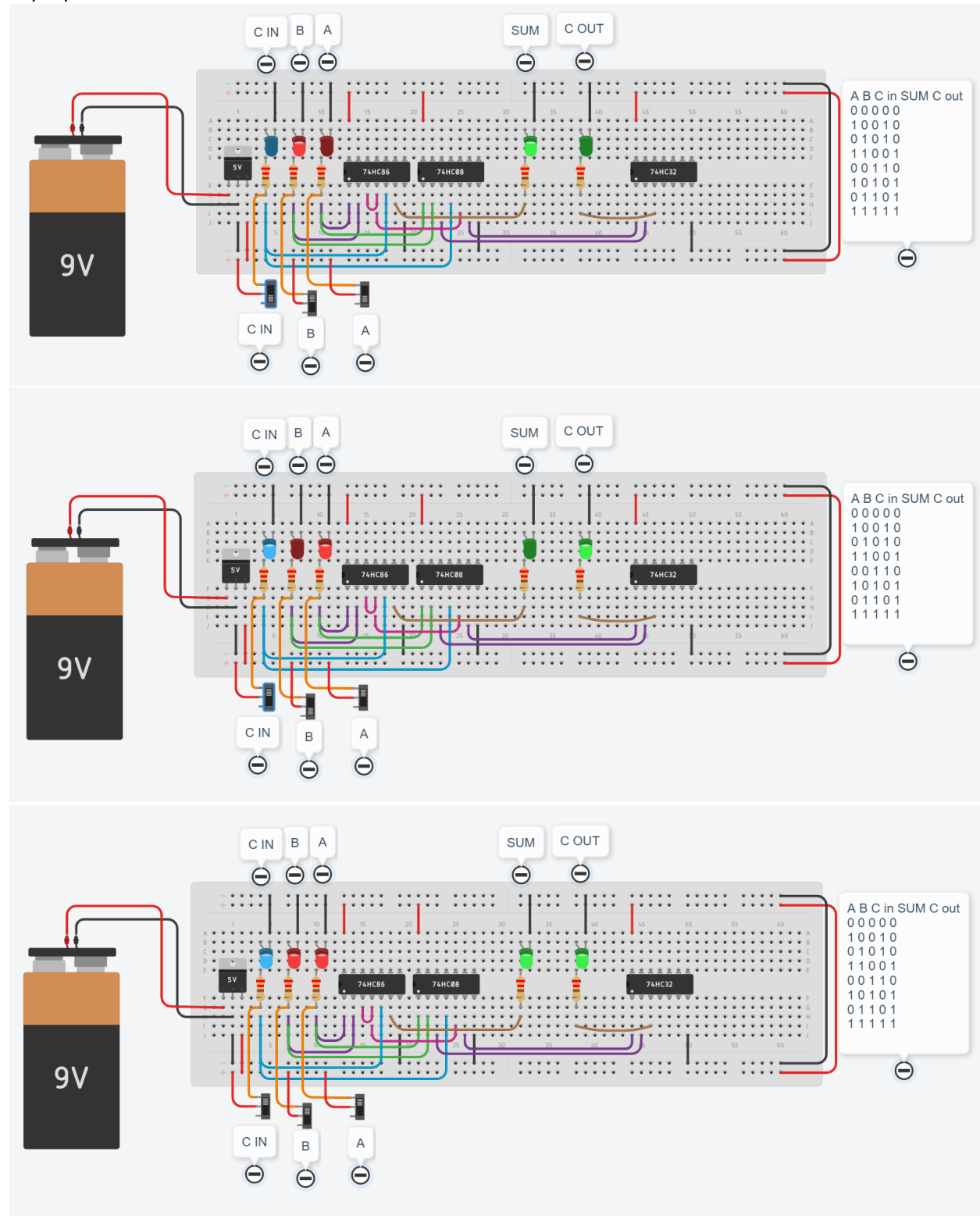Project: Full Adder
Brandon Ackerman
11/12/20



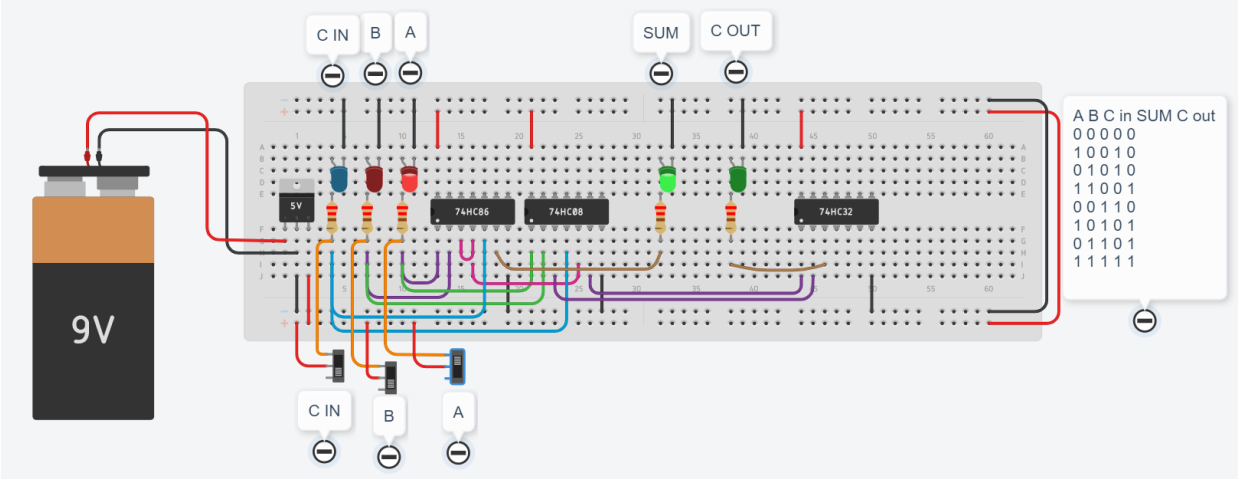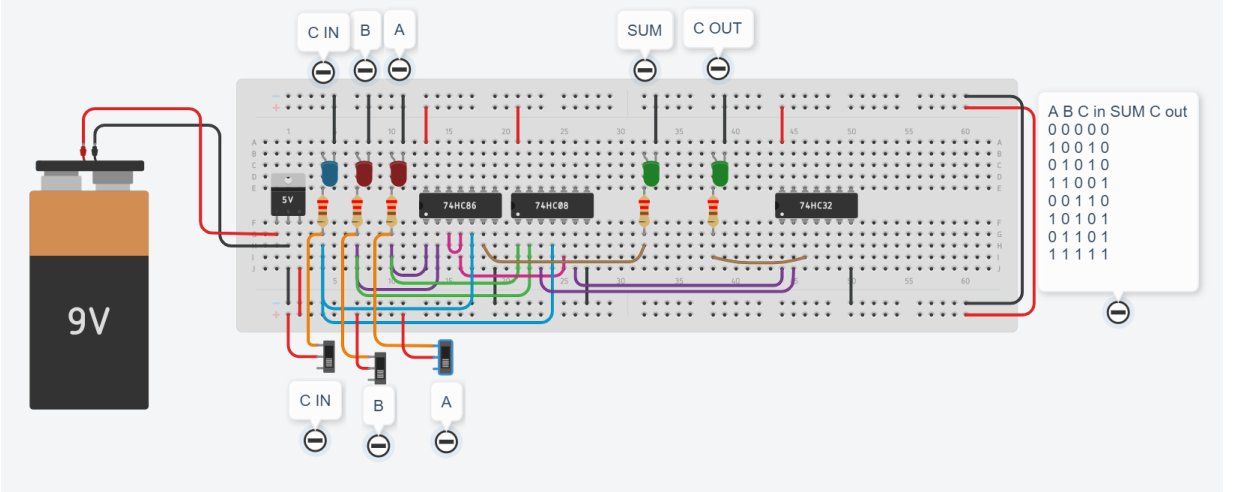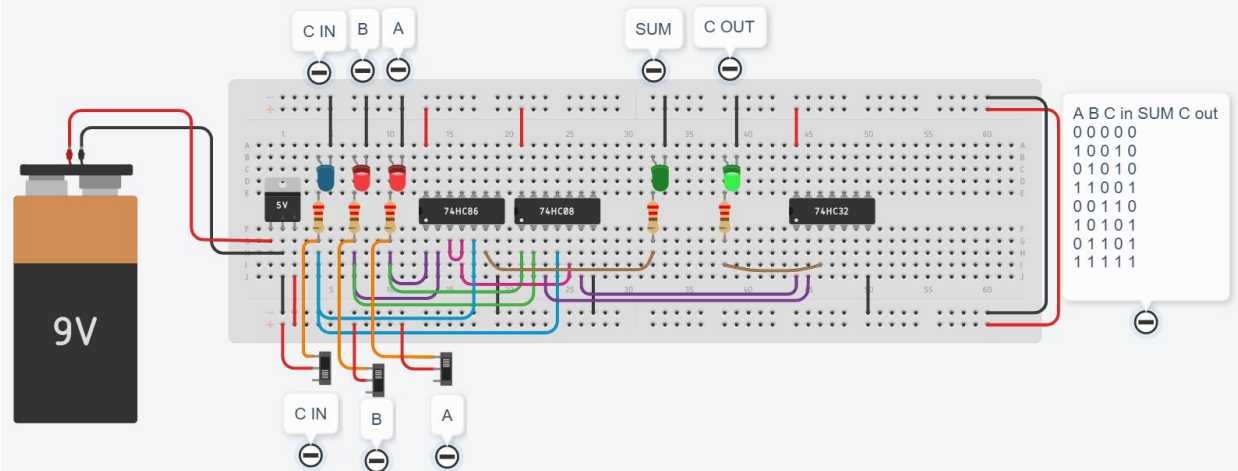Project: Full Adder
Brandon Ackerman
11/12/20



Project: Full Adder
Brandon Ackerman
11/12/20

